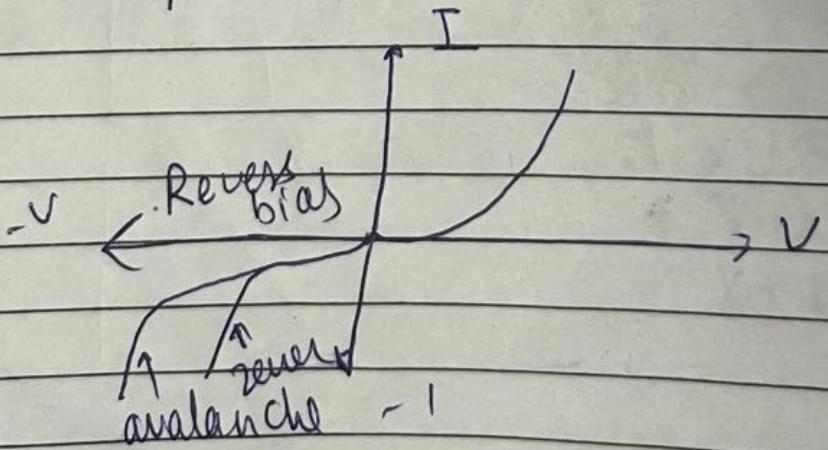


Ques Difference b/w zener and avalanche breakdown

Ans Zener

- | | |
|--|--|
| <p>① Happens at the junction which are heavily doped and have narrow depletion region</p> <p>② Has a very strong electric field in the depletion region</p> <p>③ In this there is a rupture of covalent bonds due to which electron-hole pair are generated. (Tunneling)</p> <p>④ On Inc temp. the reverse voltage inc. breakdown</p> <p>⑤ Hard characteristic no knee point</p> | <p>avalanche</p> <p>① Happen at the junction which are lightly doped and have wide depletion region</p> <p>② Doesn't have as strong electric field</p> <p>③ In this minority carriers collide with the semi conductor atoms and electron-hole pair are generated then accelerated by the electric field result in more collision</p> <p>④ On Inc temp the reverse voltage inc.</p> <p>⑤ Soft characteristic knee point</p> |
|--|--|



$$a = e^b$$

$$b = \ln a$$

DATE: _____
PAGE: _____

Ques

$$I_S = 2.2 \times 10^{-6}$$

$$T = 300$$

$$I_D = 9 \times 10^{-3}$$

$$I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} \times 300}{1.6 \times 10^{-19}}$$

$$= \frac{1.38 \times 3 \times 10^{-23+2+9}}{1.6}$$

$$k = 1.38 \times 10^{-23} \text{ J/K}$$

T = in Kelvin (300 in this)

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$= \frac{1.38 \times 3 \times 10^{-2}}{1.6}$$

$$= 2.58 \times 10^{-2}$$

$$= 0.258 \times 10^{-3}$$

$$n = 1$$

$$\frac{I_D}{I_S} = e^{\frac{V_D}{nV_T} - 1}$$

$$= \frac{9 \times 10^{-3}}{2.2 \times 10^{-6}} = \frac{4.09 \times 10^3}{4090}$$

$$4090 = e^{\frac{V_D}{0.258 \times 10^{-3}}}$$

$$\log \ln(4090) = \frac{V_D}{0.258 \times 10^{-3}}$$

$$8.3 = \frac{V_D}{0.258 \times 10^{-3}}$$

$$8.3 \times 0.258 \times 10^{-3} = V_D$$

$$V_D = 2.1 \text{ mV}$$

Jup

Sidooal


F.B (O.C)

R.B (O.C)

DATE: _____

PAGE: _____

Ques

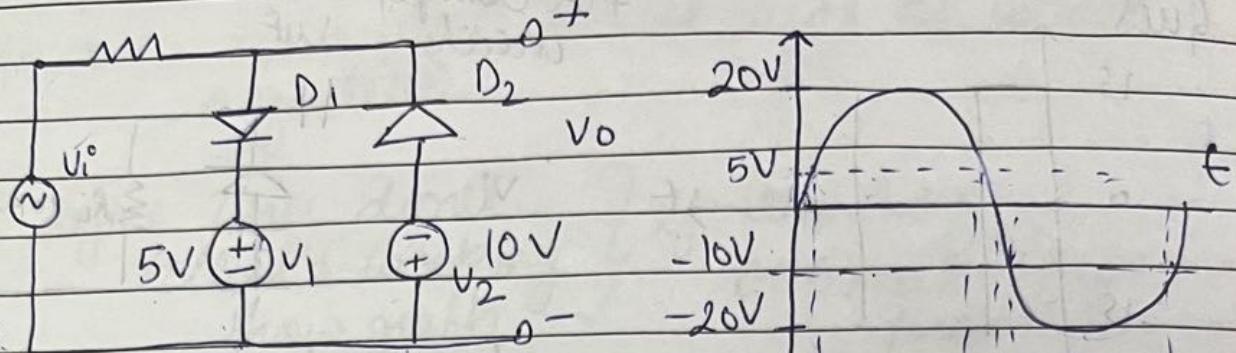

for +ve half cycle

$D_2 \rightarrow R.B$ by V_1^o, V_2 (open circuit)

$$V_i^o > 5V$$


D_1 will be forward bias by V_i^o

replace ~~open circuit~~ D_1 with $0.7V$

$$V_i < 5V$$

D_1 will be reverse bias

$D_1 \rightarrow$ open circuit

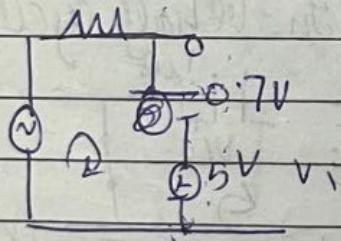

~~$5 + 0.7 - V_o = 0$~~

$$V_o = 5 + 0.7$$

$$= 5.7V$$


for -ve half cycle V_o follow V_i when $V_i < 5V$

V_o follows V_i

D_1 will be reverse bias (O.C)

$V_i > -10$, D_2 in R.B due to V_2 (O.C)

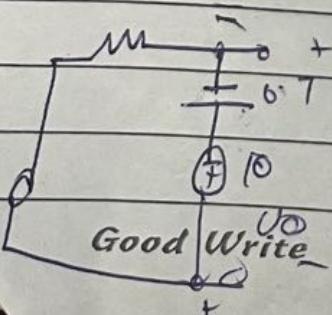
$V_i < -10$, D_2 in F.B due to V_2 (0.7V)



$$V_o = -10 - 0.7 = -10.7$$

Good Write

ques

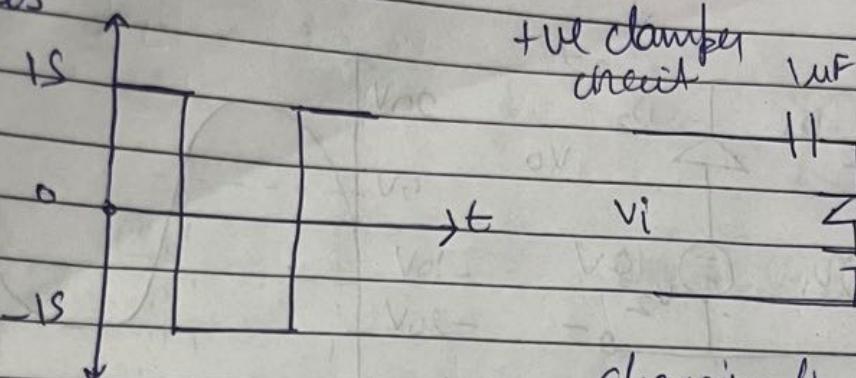

charging time const (diode)

$$T = R + C$$

$$= 0$$

discharging time const, $T = R_C$

$$= 1 \times 10^{-6} \times 10 \times 10^3$$


$$= 10\text{ms}$$

$$\text{discharging time} = T = 5R_C = 5\text{ms}$$

① analysis cycle which will put diode in F.B

+ve half cycle


diode will be reverse biased

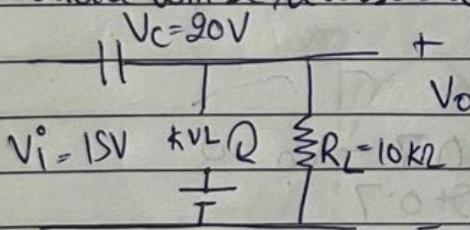

$$15 + 20 - V_o = 0$$

$$V_o = 35V$$

In - ve half cycle diode = F.B

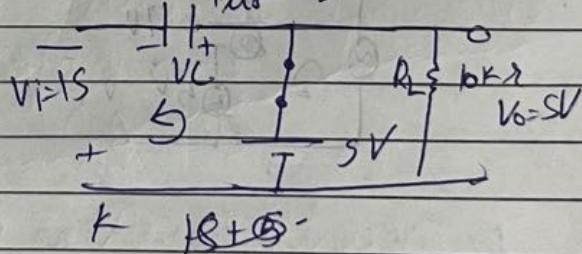

$$-15 - 5 + V_C = 0$$

$$V_C = 20V$$

(no explanation) $V_o = 5V$

Ques State and Prove De-Morgan Theorem

Aus

$$X+Y = \overline{\bar{X} \cdot \bar{Y}}$$

$$\overline{X \cdot Y} = \bar{X} + \bar{Y}$$

X	Y	\bar{X}	\bar{Y}	$X+Y$	$\overline{\bar{X} \cdot \bar{Y}}$	$\bar{X} + \bar{Y}$
0	0	1	1	1	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

equal

$\overline{X \cdot Y}$	$\bar{X} + \bar{Y}$
1	1
1	1
1	1
0	0

equal

de morgan law states that

$$\overline{X+Y} = \bar{X} \cdot \bar{Y} \quad \text{---(1)}$$

let us assume ---(1)

is true

now we try to prove
complement law

$$A + \bar{A} = 1$$

$$A = \overline{\bar{A}}$$

~~$$\bar{A} + \bar{\bar{A}} = 1$$~~

$$\overline{A+Y} + \overline{\bar{A}+Y}$$

$$\overline{A+Y} + A+Y$$

$$\overline{A \cdot Y} + A+Y$$

$$(A+Y)(\bar{Y}+A)+Y$$

$$A \bar{Y} + A+Y$$

$$A+1 = 1$$

how

$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$

$$A \cdot \overline{A} = \overline{I}$$

$$A = \overline{X \cdot Y}$$

$$\begin{aligned} & \overline{X \cdot Y} \cdot \overline{X \cdot Y} \\ &= \overline{X \cdot Y} \cdot X \cdot Y \\ &= (\overline{X} + \overline{Y}) X \cdot Y \\ &= \overline{X} + (X + \overline{Y})(\overline{Y} + \overline{Y}) \\ &= \overline{X} + (X + \overline{Y}) \cdot 1 \\ &= \overline{X} + X + \overline{Y} \\ &= I + \overline{Y} = I \end{aligned}$$

Hence proved


$$h \cdot X + \frac{h \cdot X}{1} =$$

$$\left(\frac{h}{k} + \frac{h}{k} \right) (h + k) + \frac{X}{k} =$$

$$\frac{X}{(B+X)} + \frac{X}{Y}$$

$$l = h + 1$$

Hence proved

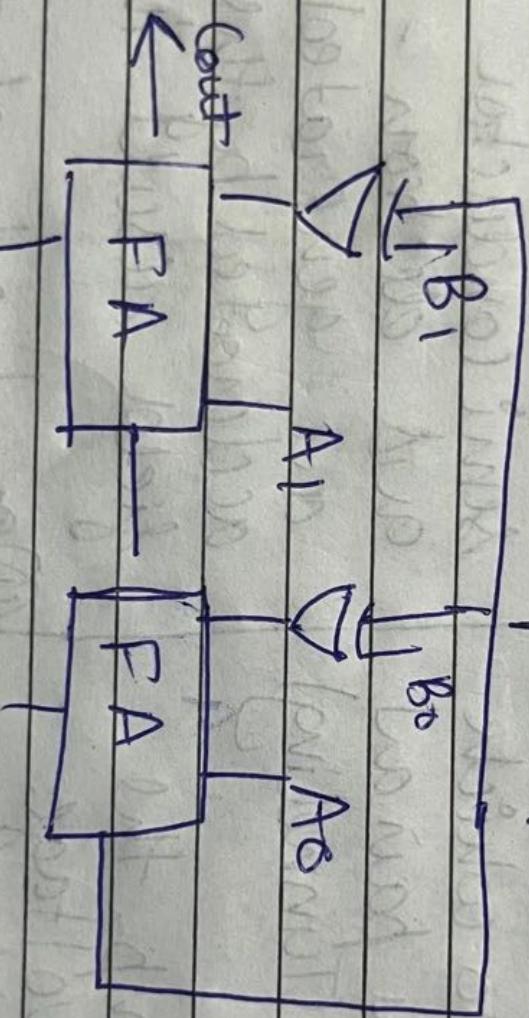

$$C = \emptyset \text{ add } C = \{\} \text{ sub}$$

S 1 S 6

Stabilization - process of making opamp

β_t independent of change
in temp changes or variation

Thermal Runaway

Flow of collector current and
also the collector leakage current
cause heat dissipation in unstabilized
circuit which leads to self
destruction

I_C inc

$$P = 1.2V$$

Stabilizat

$|CBO$

P_{DC}

V_{BE}

Voltage divider biasing

3. β

$$S(\beta) = \frac{\Delta I_C}{\Delta B} \quad \text{double for } 10^\circ C, \text{ In}$$

Ques what is thermal runaway
 I_{CBO}, C

$$k = \alpha I_B + I_{CBO}$$

as temp in I_{CBO} inc

I_{CBO} inc I_C inc

$$P = I^2 R$$

so more power dissipation

To prevent use heat sink

Early effect is main limitation of BJT
disadv


1. Bulky
2. Noisy
3. thermal runaway
4. leakage current at high freq.

Adv

1. large gain bandwidth
2. low forward vol. drop
3. low off impedance high ip impedance
4. long life

COMMON Emitter

→ Most Common Configuration.

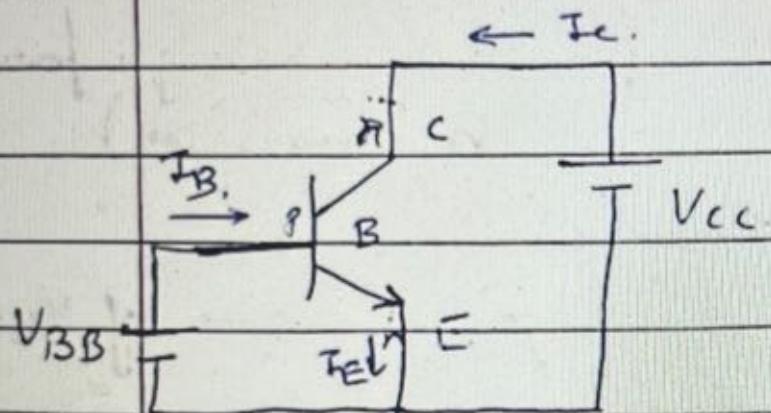


npn CE

For active region $V_{BB} < V_{CC}$


I_B characteristics

I_B vs V_{BE} for diff values

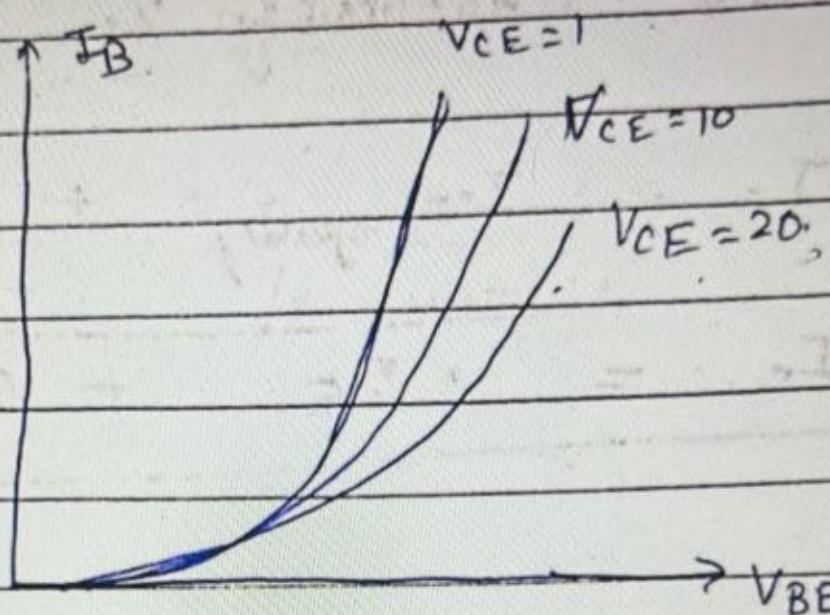


- I/P characteristic quite similar to F-B.
- In comparison with CB, current less rapidly increases with increase in V_{BE} .
This means i/p impedance is high for CE. (Details during h-parameter)
- As the $V_{CE} \uparrow$

- V_{BE}
- I/P characteristic quite similar to F-B.
 - In comparison with CB, current less rapidly increases with increase in V_{BE} . This means i/p impedance is high for CE. (Details during h-parameter)
 - As the $V_{CE} \uparrow$ I_B decreases for a value of V_{BE} .
 - Why? With increase in V_{CE} , the effective reverse ~~V_{EB}~~ voltage is increased b/w B & C, Depletion layer widen, Base width reduces, so less base current.

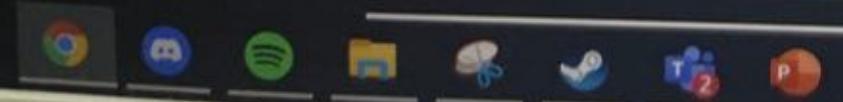

~~O/P~~ O/p Characteristics.

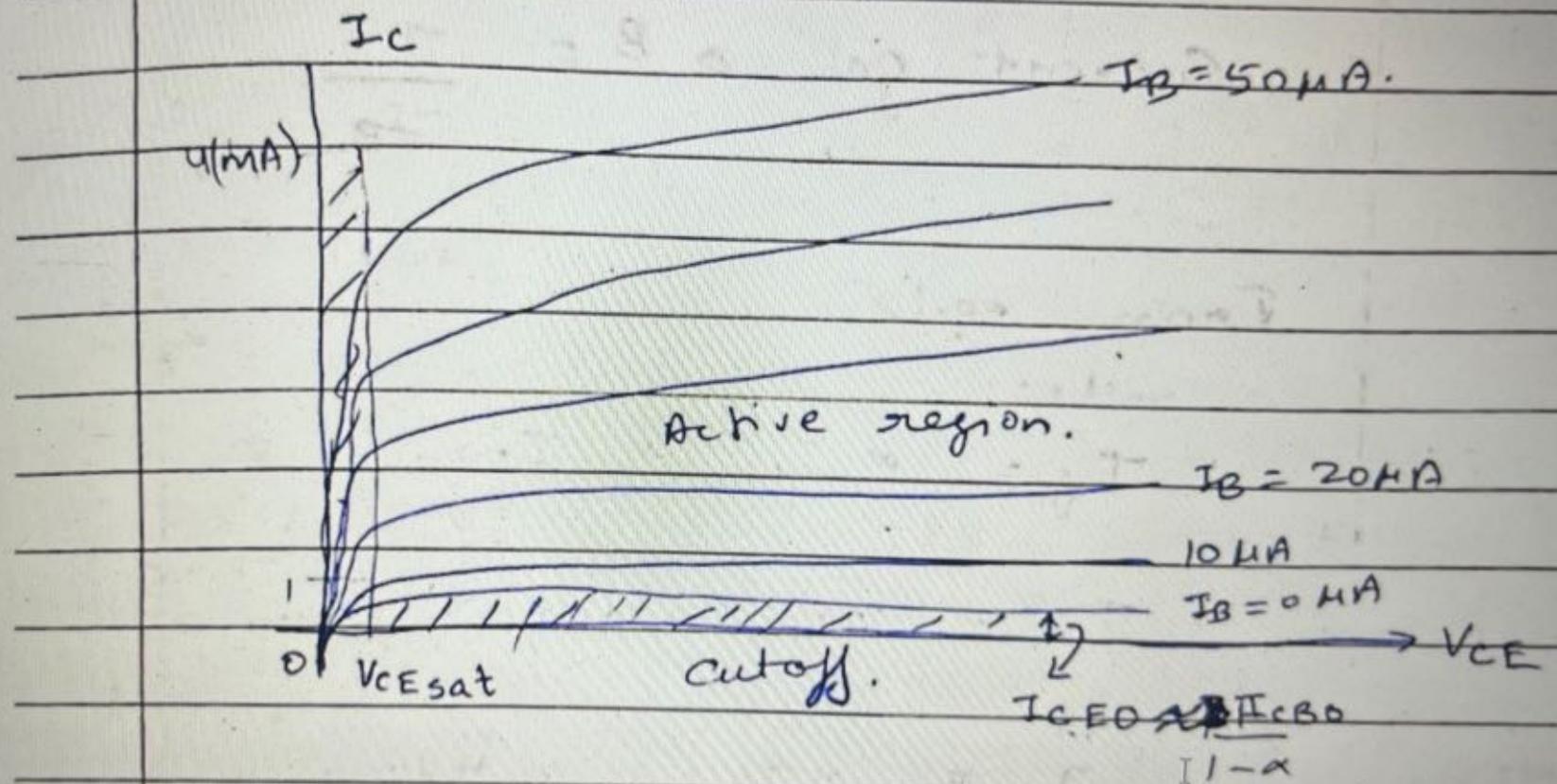

By ~~es~~ Comparison with CB O/p characteris.

→ Slope is ~~high~~

why

Page 18 / 58 - Q +

It offers less o/p resistance.

By co Comparison with CB O/p characteristics

→ Slope is high.

why → It offer less o/p resistance.

I_{CEO} = current when i/p is open circuit, i.e $I_B=0$.

here I_{CEO} is much higher than I_{CBO} .

Details after B)

Definition : For ~~more amplification purpose~~ ~~circuit~~
~~region~~ ~~cutoff region~~ for CE, the I_C current can be defined as.

From eq.(2)

$$I_c = \alpha I_E + I_{cBO}$$

$$I_c = \alpha (I_e + I_B) + I_{cBO}$$

$$I_c = \alpha I_e + \alpha I_B + I_{cBO}$$

$$(1-\alpha) I_e = \alpha I_B + I_{cBO}$$

$$I_e = \frac{\alpha I_B + I_{cBO}}{1-\alpha}$$

I_c at $I_B=0$ is I_{cBO}

$$I_{cFO} = \frac{I_{cBO}}{1-\alpha}$$



$I_B = 0 \text{ mA}$

Common Emitter Configuration

ASET

In common emitter configuration, base is the input terminal, collector is the output terminal and emitter is the common terminal for both input and output.

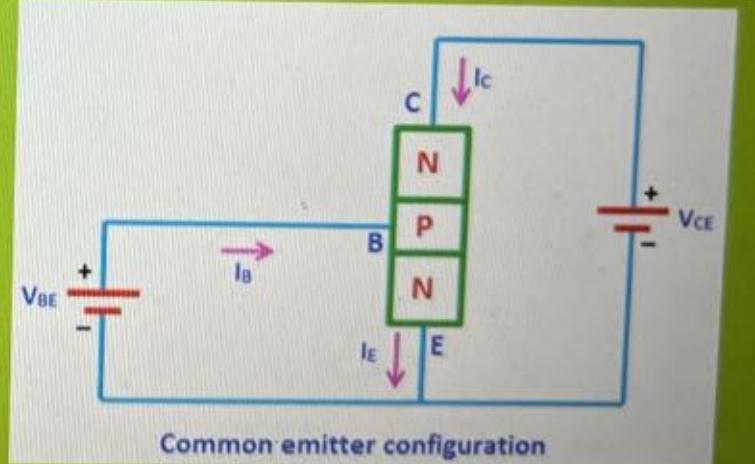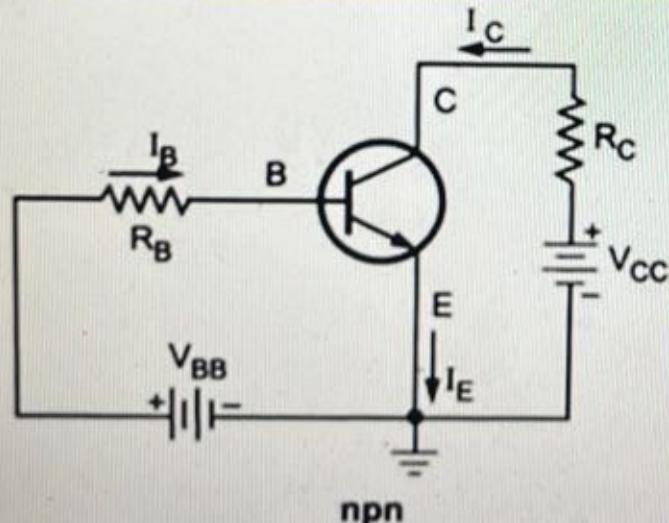Thus the Emitter terminal of a transistor is common for both input and output terminals and hence it is named as **common emitter configuration**.





Be careful—files from the Internet can contain viruses. Unless you need to edit, it's safer to stay in Protected View.

Enable Editing

AMITY
UNIVERSITY

ASET

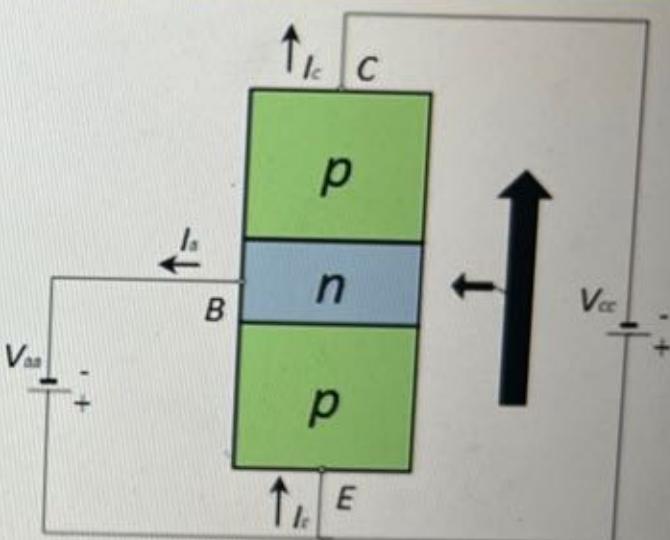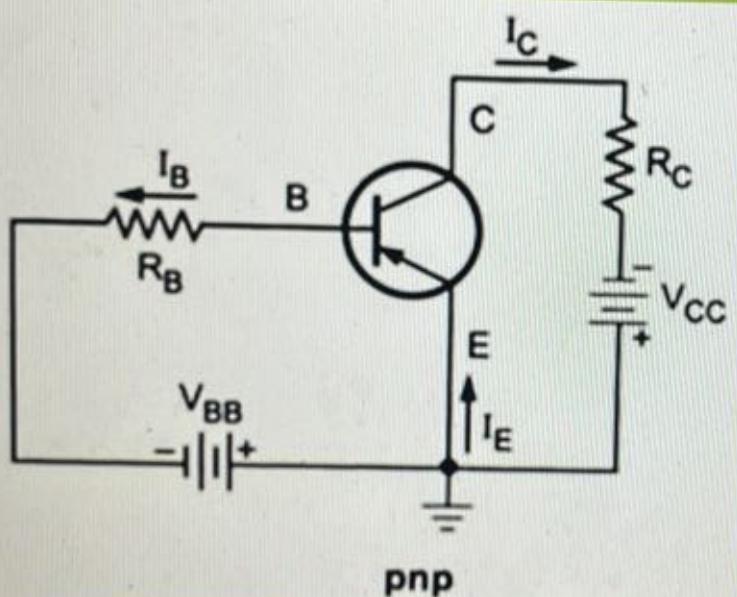


Input characteristic

ASET

The curve plotted between input current and the input voltage by keeping the output voltage constant is called input characteristics.

Input current-Emitter current I_B
Input Voltage- Emitter-Base voltage V_{BE}
Output Voltage - V_{CE}
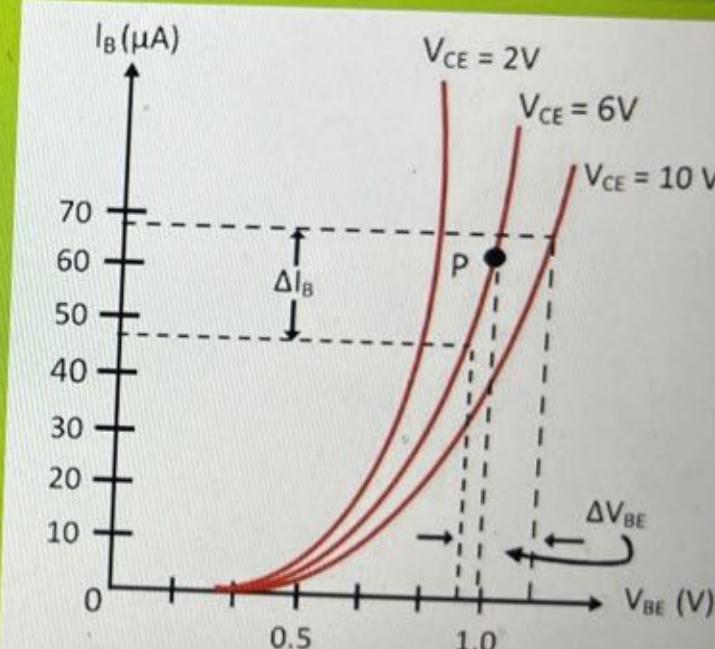
$$r_i = \frac{\Delta V_{BE}}{\Delta I_B} \text{ at constant } V_{CE}$$




Output Characteristic

ASET

The characteristic curve which is plotted between output current and output voltage by keeping the input current constant is called output characteristic. Also called as collector characteristics.

Output current-collector current I_C
Output voltage- collector-Base voltage V_{CE}
Input current - I_B
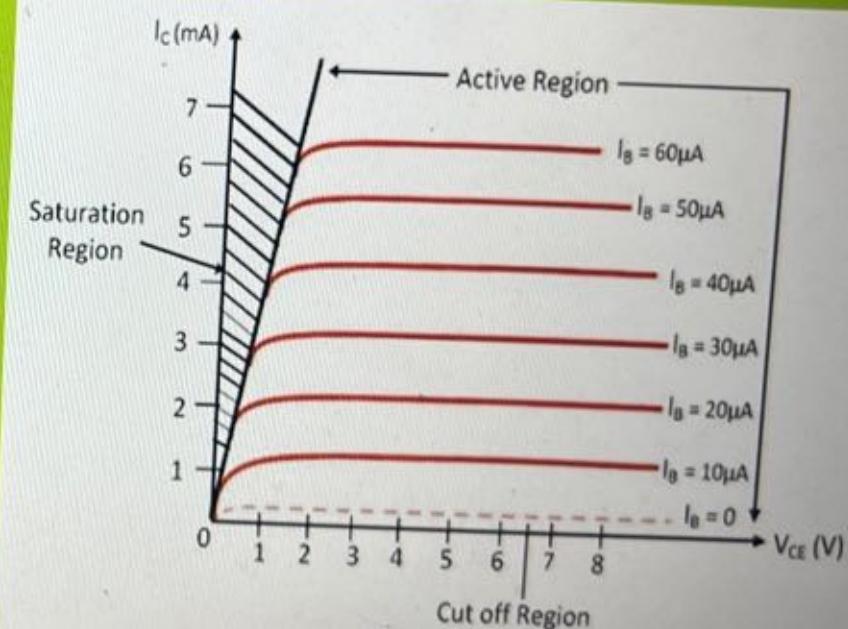
$$r_o = \frac{\Delta V_{CE}}{\Delta I_C} \text{ at constant } I_B$$



$$V_{CE} - I_C R_C - V_{CE} - I_E R_E = 0$$


$$V_{CE} = V_{CC} - I_C R_C - I_E R_E \\ = 10 - I_C (R_C + R_E)$$

$$= 10 - 100 \times \frac{3.58 - 0.7}{0.2 + 101 \times 0.56} (1 + 0.8)$$

$$A_{vS} = -$$

Ques

Common source JFET amplifier.

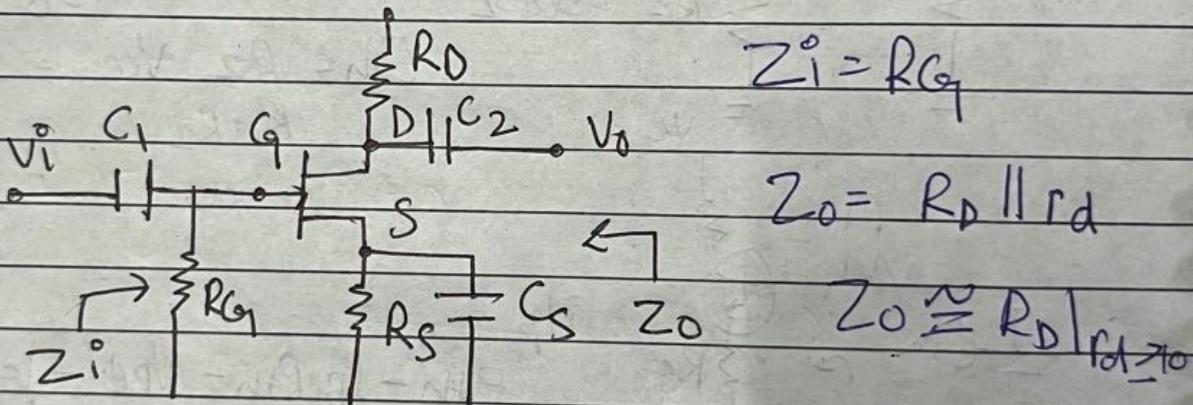

$$A_v = -g_m (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = -g_m R_D$$

$r_d > 10 R_D$

~~$R_D \neq g_m R_S$~~

$$1 + g_m R_S$$

$$A_v = \frac{g_m R_D}{1 + g_m R_S}$$

Ques Prev year r_d not given

$$A_V = \frac{gm r_D}{1 + gm r_S} \quad \text{--- (1)}$$

$$\begin{aligned} r_D &= R_D || R_L \\ &= 6k || 10k = 3.75k\Omega \end{aligned}$$

$$r_S = R_S = 4000\Omega$$

$$\therefore A_V = \frac{4000 \times 10^{-6} \times 3.75 \times 10^3}{1 + 4000 \times 10^{-6} \times 400}$$

$$A_V = 5.7$$

$$\begin{aligned} \text{if } r_S &= 0 \\ A_V &= gm r_D = 400 \times 10^{-6} \times 3.75 \times 10^3 \\ &= 15 \end{aligned}$$

H-channel depletion region \rightarrow working (3 mode)

$$200\text{mV} = \left(\frac{-400}{4k} \right) = -100$$

$$v_o = \frac{(-100) \times (0.2)}{1k} = -0.20 \text{ V}$$

$$R_1 = \infty$$

$$R_C = 0$$


$$Z_i = \left(\frac{0.2}{4 \times 10^3} \right) = 0.05 \text{ m}\Omega$$

amplifier has
determine the ampli-

Ques Show how zener diode can be used as voltage regulator.

Ans Define zener diode if compulsory tell it's working or 5 mark above show graph question

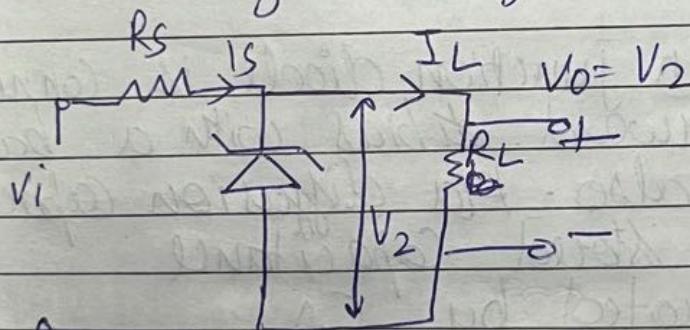Zener diode are widely used as shunt voltage regulator for small load. This is done by attaching it parallelly to the load. The Breakdown voltage remain const. for variety of current. We attach it such a way that it remains in reverse bias. When Zener diode voltage exceed knee voltage voltage become const.



Ques designing voltage regulator $V_0 = 30V$ $R_L = 1.2K\Omega$
 $V_i = 40V \sim 60V$

R_s , I_L and I_m

Ans $V_0 = V_L = 30$

using voltage divider rule on V_i

$$V_0 = R_L V_i \frac{R_s}{R_L + R_s} \frac{1200 \times 40}{1200 + 30}$$

$$1.2 - 1.2 \\ = 0.4K\Omega$$

$$30 = 1.2K \times 40$$

$$R_s = \frac{30}{1200} \times \frac{30}{3}$$

$$1.2K + R_s = 400 \times 4$$

$$R_s = 3.33K\Omega$$

Good Write

for I_L

$$I_{Rs} = \frac{V_i - V_L}{R_s}$$

$$= \frac{60 - 30}{\cancel{0.4}} = \frac{30}{\cancel{0.4} \times K_2} = \frac{30 \times 10^{-3}}{0.4} = 75 \text{ mA}$$

$$I_L = V_L = \frac{30}{R_L} = \frac{1 \times 10^{-1}}{120 \times 10^3} = 0.025 \text{ A} \\ = 25 \text{ mA}$$

for I_{ZM}

$$I_{Zm} = I_{Rs} - I_L \\ = 75 - 25 \text{ mA} \\ = 50 \text{ mA}$$

ques Diffusion capacitance

Ans When a p-n junction diode is connected in forward bias with a battery it is also known as diffusion capacitance or stored capacitance denoted by C_D

It occurs due to stored charge of minority charge carriers holes in p-side & holes in n-side.


It is very dense near the junction. The density decreases as distance increases.

It is more than transition

capacitance

$$C_D = \frac{i T}{n V T}$$

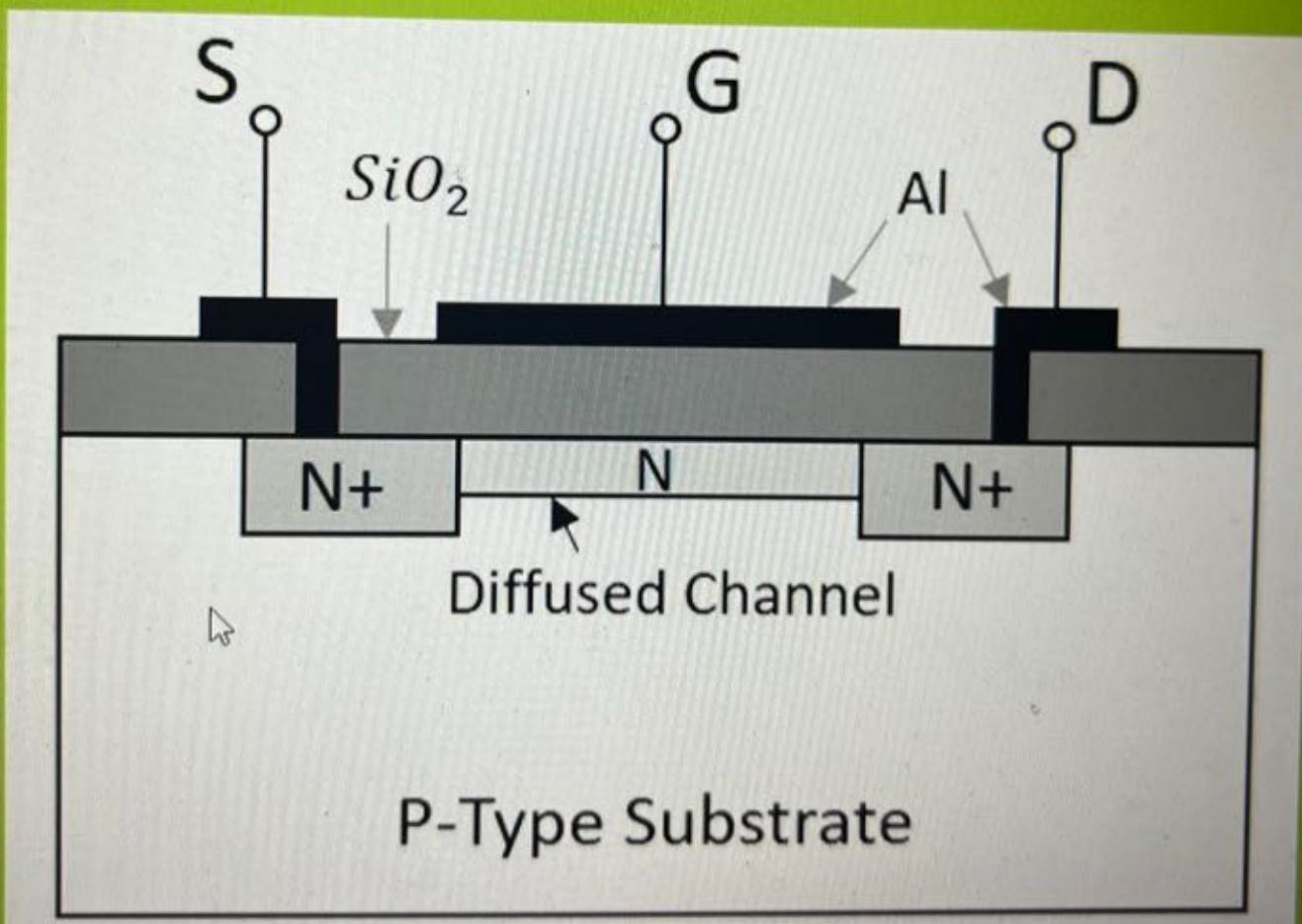Construction of N-channel Depletion MOSFET




P-type substrate is taken into which two heavily doped N-type regions are diffused, which ac-



Depletion-Type MOSFET Construction


DE-MOSFET

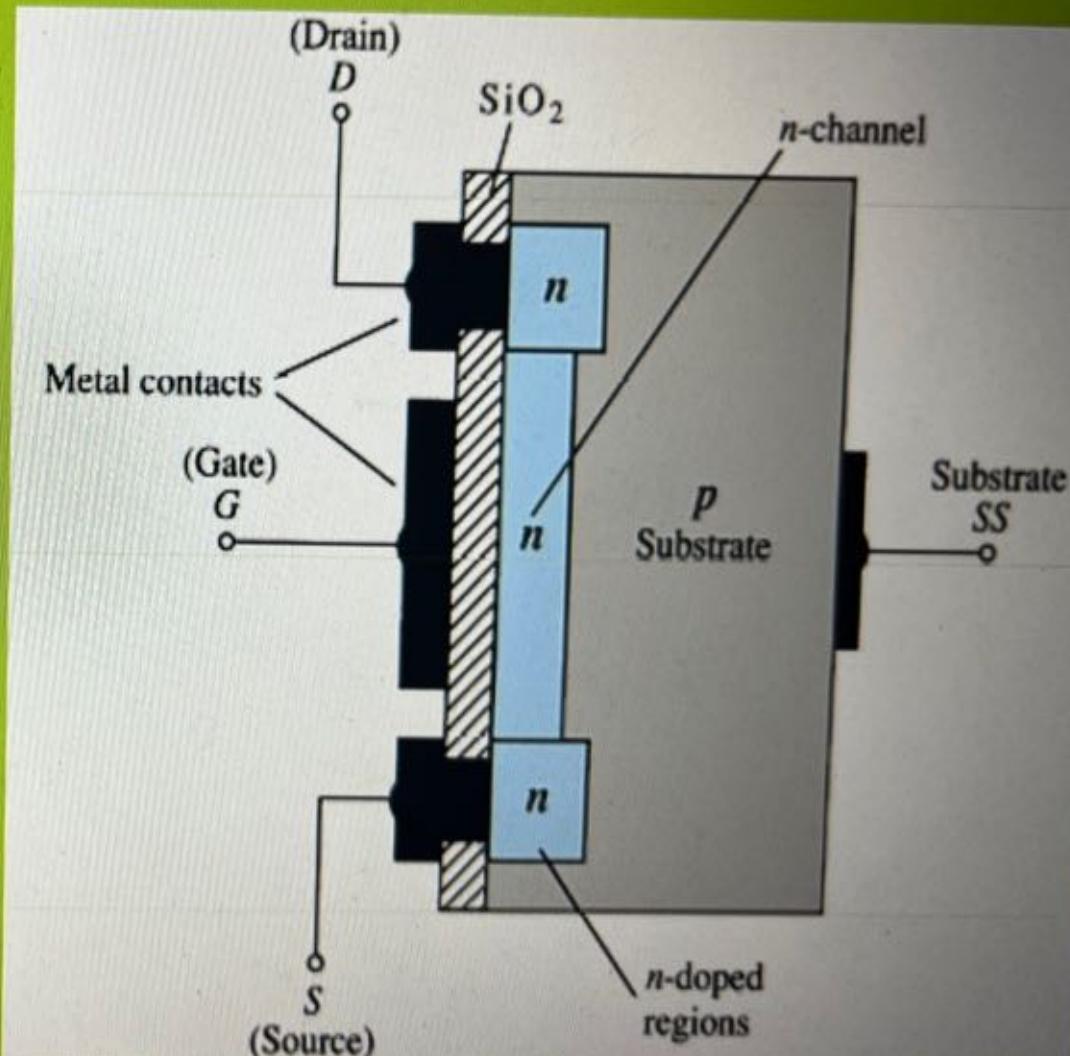The Drain (D) and Source (S) connect to the two *n*-doped regions. These *n*-doped regions are connected via an *n*-channel. This *n*-channel is connected to the Gate (G) via a thin insulating layer of SiO_2 .



Depletion Type MOSFET.

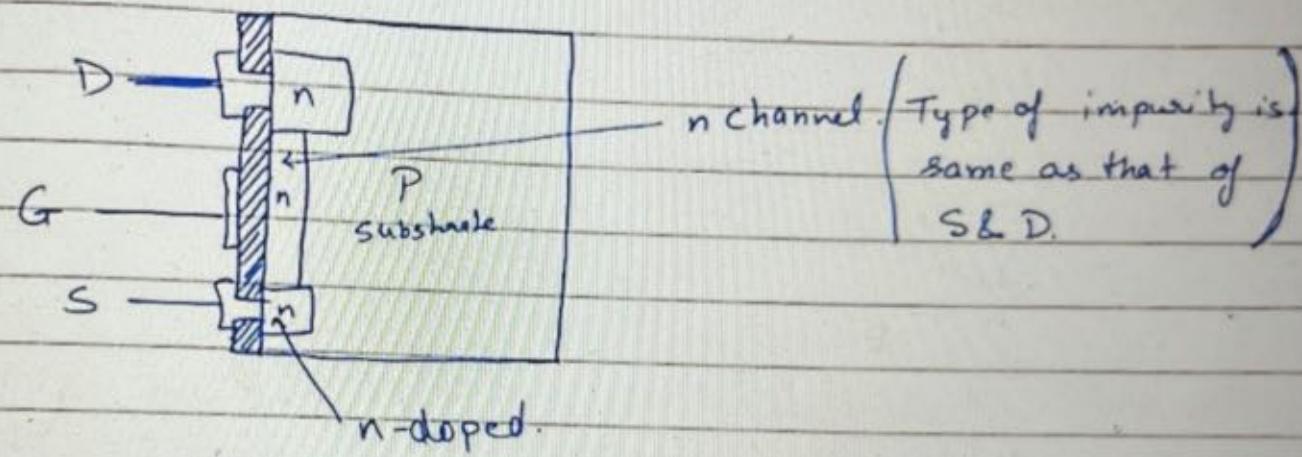→ Same structure with one ~~one~~ addition.
n-channel adjacent to SiO_2



Operation

→ Like JFET.

$$V_{GS} = 0$$

$$V_{DS} = +ve$$

current flow.

$$V_{DS} = \uparrow$$

current reach

Operation

→ Like JFET.

$$V_{GS} = 0$$

$$V_{DS} = +ve$$

current flow.



$$V_{DS} = \uparrow$$

current reach
saturation because
of pinch-off


→ As $V_{GS} \uparrow$ pinch-off occur on higher value of V_{DS} .

→ $V_{GS} \downarrow$ pinch-off occur at lower values of V_{DS} .

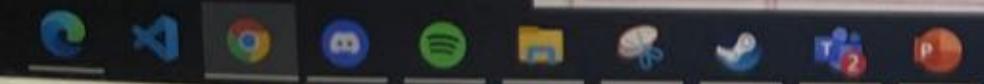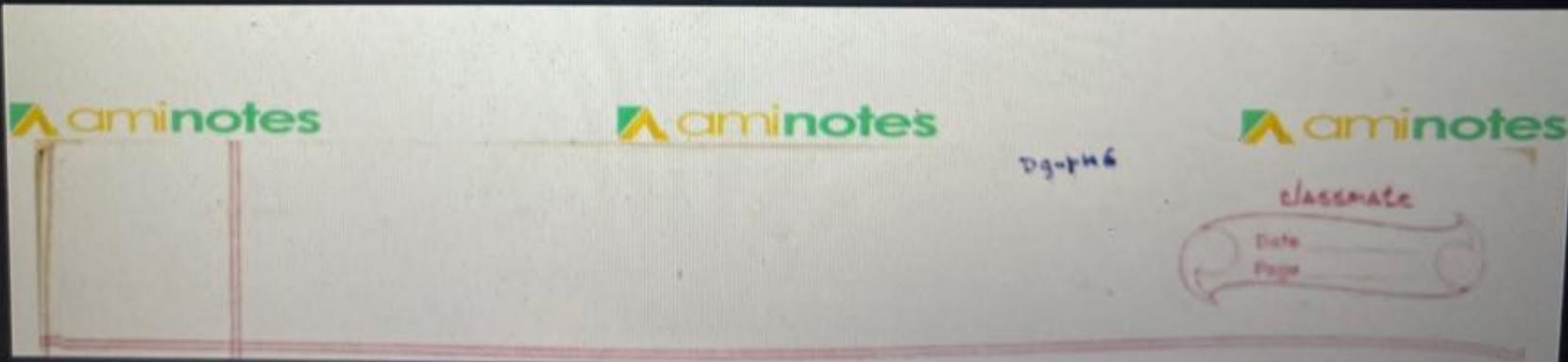→ $V_{GS} < 0$, For -ve value, e^- get repelled and
at $V_{GS} = V_p$ (a negative value)



Characteristic Curve.

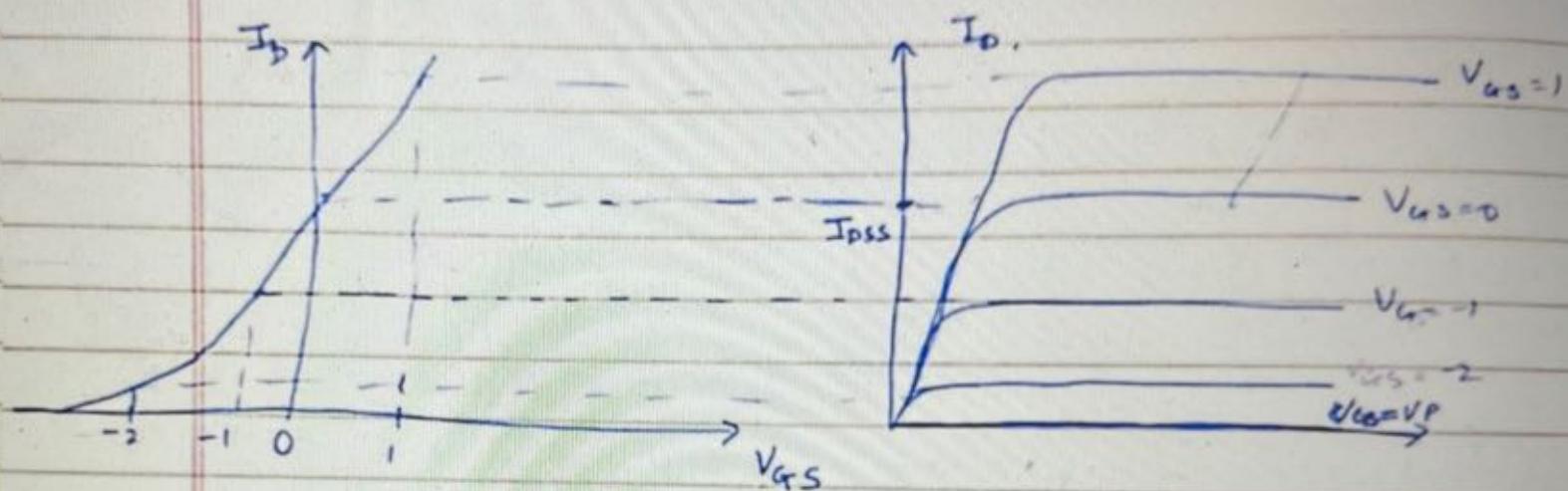

Equation: Same as that of JFET

Shockley's equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$