

Roll No.

Total Pages : 3

305504

December, 2019

**B.Tech. (ECE) - V SEMESTER
CMOS Design (ECEL501)**

Time : 3 Hours]

[Max. Marks : 75

Instructions :

1. It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.
2. Answer any four questions from Part-B in detail.
3. Different sub-parts of a question are to be attempted adjacent to each other.

PART - A

1. (a) Differentiate between MOS as resistance and MOS as current source configuration. (1.5)
- (b) What is threshold voltage of MOS device? (1.5)
- (c) Why selection of W/L ratio of a MOS device is critical? (1.5)
- (d) What is the impact of channel length modulation on drain current? (1.5)

305504/210/111/405

[P.T.O.
16/12

- (e) What is difference between layout and stick diagrams? (1.5)
- (f) What is velocity saturation effect? (1.5)
- (g) Design two input or gate using pseudo inverter configuration. (1.5)
- (h) What is the meaning of scaling of MOS devices? (1.5)
- (i) How subthreshold conduction of MOSFET can be advantageous? (1.5)
- (j) How junction leakage of a MOS device can be reduced? (1.5)

PART - B

- 2. (a) Describe twin tub process for fabrication of the CMOS transistor with suitable diagram. (10)
- (b) Explain VLSI design flow with suitable flow chart. (5)
- 3. (a) Explain various regions of operation for NMOS. Derive the expression for the drain current in various region of operation for NMOS. (8)
- (b) Explain RC delay model and linear delay model of CMOS circuits. (7)

- 4. (a) What is transmission gate logic? Why it is preferred over NMOS/PMOS switch? Design 4×1 Mux using transmission gate logic. (8)
- (b) Using an example enlist the various steps for designing a sequential CMOS logic circuit. (7)
- 5. (a) What is the rise time and fall time of CMOS inverter? Explain using necessary expression. (8)
- (b) Explain the static and dynamic power dissipation in CMOS circuits with necessary diagram and expression. (7)
- 6. (a) Explain the operation of CMOS dynamic logic. What is the cascading issue in dynamic logic circuits? (8)
- (b) What is NMOS inverter? Explain the different form of pull up. (7)
- 7. (a) What is latch up? How it can be reduced? (5)
- (b) Draw circuit and stick diagram for half subtractor using CMOS combinational logic design. (10)