

5. (a) Explain the working of ECL by making a NOR gate through it. 5
- (b) Implement Ex-NOR, NAND and NOR gate using CMOS Logic. 5
- (c) What precautions are necessary for handling MOS devices ? 5
6. (a) Explain the working and advantages of Successive approximation register type ADC. 5
- (b) Why is it difficult to build an accurate 8-bit binary-weighted D/A converter ? 5
- (c) How Single-Slope and Dual-Slope ADC differs ? Discuss advantage and disadvantage of both. 5
7. (a) Implement the full adder circuit using PLA by deriving the PLA programming table. 10
- (b) How does a programmable logic device differ from a fixed logic device ? What are the primary advantages of using programmable logic devices ? 5

Roll No. 23001017055

Total Pages : 04

017301

December 2024

B. Tech. (EEIoT) (Third Semester)

Digital Electronics (EEN-301)

Time : 3 Hours]

[Maximum Marks : 75

**Note :** It is compulsory to answer all the questions (1.5 marks each) of Part A in short. Answer any *four* questions from Part B in detail. Different sub-parts of a question are to be attempted adjacent to each other.

#### Part A

1. (a) Describe the function of pull-up resistor when it is used with an open-collector TTL output. 1.5
- (b) How many BCD bit are required to drive a 3-digit thermometer display ? 1.5
- (c) Give the equivalent of decimal number 297 in the following : 1.5
- (i) Excess-3 Code
- (ii) BCD
- (iii) Hexadecimal.



- (d) Which logic family offers the fastest speed ?  
What is the parameter which supports this behaviour ? 1.5
- (e) What is the maximum possible number of states in a ripple counter consisting of 5 flip-flops ? 1.5
- (f) How does a synchronous counter differ from an asynchronous counter ? 1.5
- (g) Draw diagram of full adder. 1.5
- (h) Give the characteristic equation of J-K flip-flop. 1.5
- (i) What are the uses of PAL ? 1.5
- (j) A 10-bit DAC has a step size of 10 mV. Determine the full-scale output voltage and the percentage resolution. 1.5

### Part B

2. (a) Minimize the following using Quine Mcluskey method :

$$f(A, B, C, D) = \pi M (1, 2, 3, 7, 8, 11, 12, 15) + d(0, 4, 14). \quad 10$$

- (b) The decimal number 6 is to be transmitted using a Hamming error correcting code : 5
- (i) What are the values of  $P_1 P_2 P_3$  ?
- (ii) What 7-digit binary number is transmitted ?
- (iii) If the binary number 1100111 is received, how can the location of error be determined ?

3. (a) Implement the following Boolean function using an 8 : 1 multiplexer considering D as the input and A, B, C as selection lines :

$$F(A, B, C, D) = AB' + BD + B'CD'. \quad 10$$

- (b) With the help of a truth table, briefly describe the functioning of a 10-line to four-line priority encoder with active LOW inputs and outputs and priority assigned to the higher-order inputs. 5

4. (a) Design a counter for the following irregular binary count sequence using 'T flip-flops':

$$001 \rightarrow 010 \rightarrow 101 \rightarrow 111 \rightarrow 001(\text{recycles}). \quad 10$$

- (b) Design S-R flip flop using J-K flip-flop. 5