

END TERM EXAMINATION**THIRD SEMESTER [BCA] JANUARY 2024****Paper Code: BCA-203****Subject: Computer Organization and Architecture****Time: 3 Hours****Maximum Marks: 75****Note: Attempt five questions in all including Q.No. 1 which is compulsory. Select one question from each unit.**

- Q1 Attempt the following (any five) [5x5=25]**
- What are logic gates? Draw the schematic diagram of XOR gate. Give its truth table.
 - Draw a MUX using NAND gates which selects from four inputs A0 to A3 and two select inputs S0 and S1.
 - What is the role of stack pointer in computer organization?
 - What is ROM? How PROM, EPROM and EEPROM differ from each other?
 - Design and explain Ring counter.
 - Explain the edge triggered D flip-flop.

UNIT-I

- Q2**
- What are Universal gates? Explain how basic gates can be realized using NAND and NOR gates. [6.5]
 - State and prove Associative and Distributive theorems. [6]
- Q3**
- Draw a full subtractor circuit using NAND gate. [6.5]
 - Minimise the following Boolean function using K-map. [6]
 $F(A, B, C, D) = \Sigma (3, 4, 5, 7, 9, 13, 14, 15)$

UNIT-II

- Q4**
- Realize JK flip-flop using SR flip flop. [6.5]
 - Differentiate between flip-flop and latches. [6]
- Q5**
- Describe the operation of PISO shift register with the help of block diagram. [6.5]
 - Differentiate Combinational and Sequential circuits? [6]

UNIT-III

- Q6**
- What is instruction cycle? Draw detailed flowchart of the instruction cycle. [6.5]
 - What are CPU buses and Why they are important? [6]
- Q7**
- Explain the different types of addressing modes in basic computer. [6.5]
 - What is a register in a CPU and How Does it Work? [6]

UNIT-IV

- Q8**
- Write difference between Programmed Input /Output and Interrupt Driven Input/output [6.5]
 - How DMA controller communicates and transfers data between peripheral devices and RAM [6]

P.T.O.

